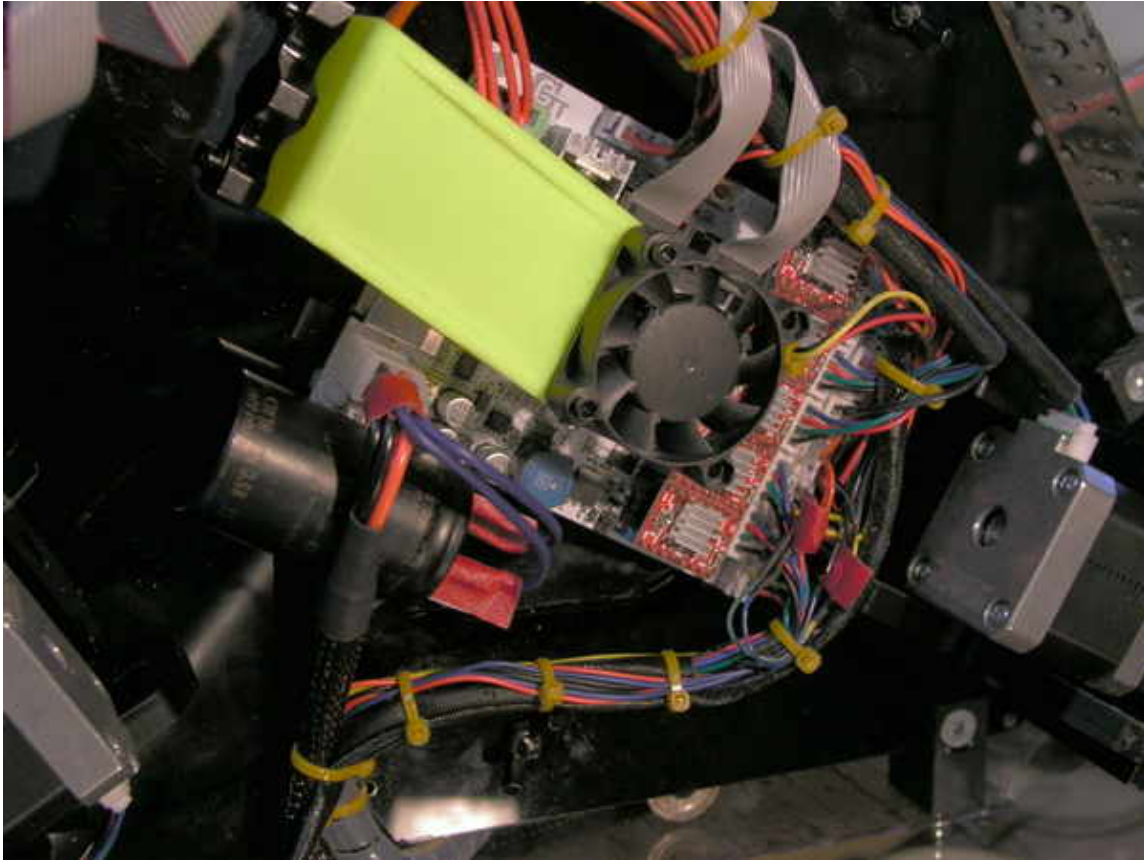




## Power surge protection capacitor to prevent printer crashes

Tue Jan 2 13:23:41  
2018

Adresse: <http://bechele.de/pages/english/129-0.html>  
Autor: Rolf Jethon



I noticed that my printer crashed from time to time for example if I switched on the light (neon tube) in the room, or when I switched on a foreign PC. This is of course annoying, if your 5 hour print is interrupted just before finishing. So I added an extra 10000  $\mu\text{F}$  Elco to the power input. Since then the described problems are gone. Probably 4700  $\mu\text{F}$  are already enough.

See the wiring:

[wiring.png](#)